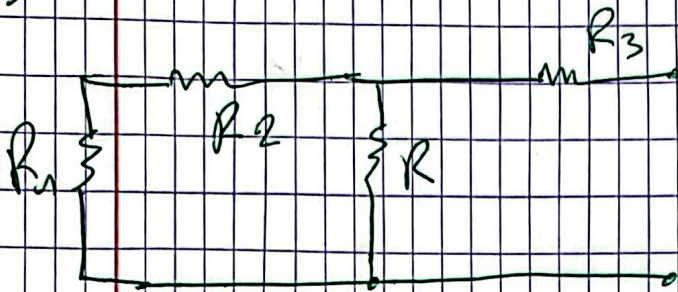


Ex 1, ~~5-13~~

3) $R_{th} = ?$ (Éteindre E et II)




méthode 1 :

$$R_{th} = \left[(R_1 + R_2) // R \right] + R_3$$

$$= \frac{(R_1 + R_2)R}{R_1 + R_2 + R} + R_3 \quad (1)$$

méthode 2

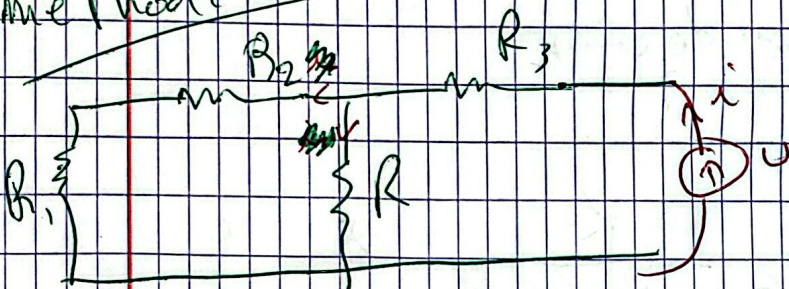



$$R_{th} = \frac{U}{i}$$



$$i = \frac{U}{R_{eq} + R_3} \Rightarrow R_{th} = \frac{U}{\frac{U}{R_{eq} + R_3}} = R_{eq} + R_3$$

$$E_{rlh} = E_1 + E_2$$


$$\underline{E_1 = ?}$$

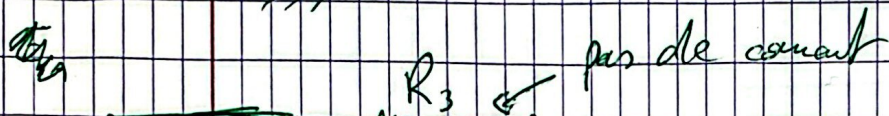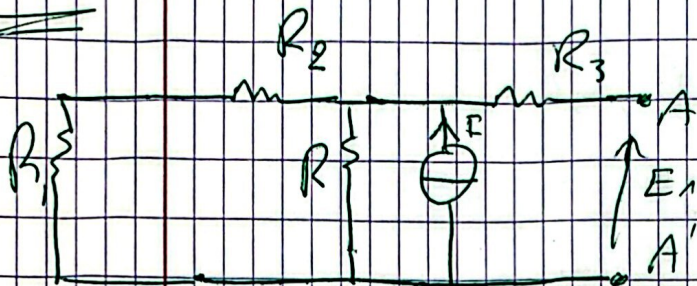

$$E_1 = R_{eq} I = \frac{(R_1 + R_2) R}{R_1 + R_2 + R} \cdot I$$

$$E_1 = \frac{(R_1 + R_2) R}{R_1 + R_2 + R} I$$

$$\underline{E_2 = ?}$$

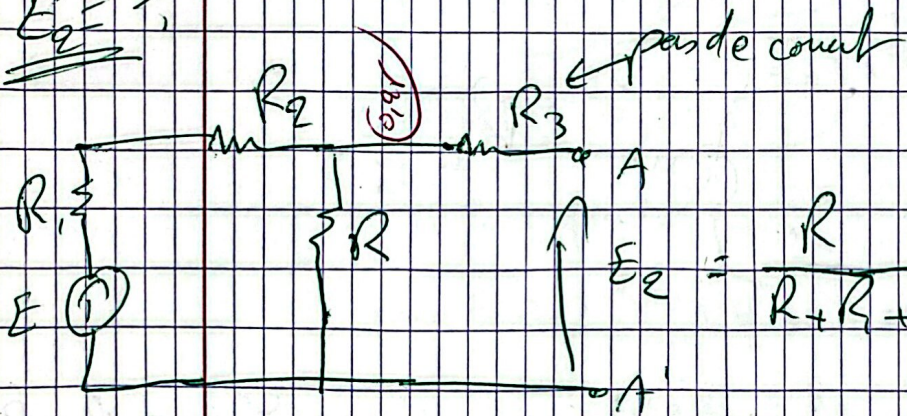


$$E_2 = \frac{R}{R + R_1 + R_2} E$$

$$\Rightarrow E_{rlh} = \frac{R}{R + R_1 + R_2} E + \frac{R(R_1 + R_2)}{R_1 + R_1 + R_2} I$$


$$R_{th} = R_{th} \text{ (1)} = R_3 + \frac{R(R_1 + R_2)}{R + R_1 + R_2}$$
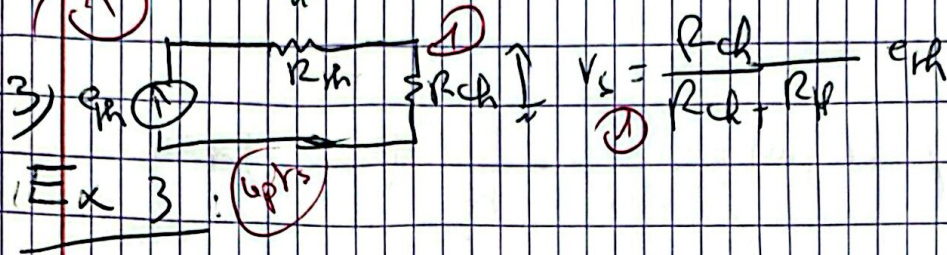
$$I_N = \frac{E_{th}}{R_{th}} = \left(R_3 E + R(R_1 + R_2) I \right) \propto \frac{1}{R_3(R_1 + R_2) + R(R_1 + R_2)}$$



$$V_s = V_{s1} + V_{s2}$$

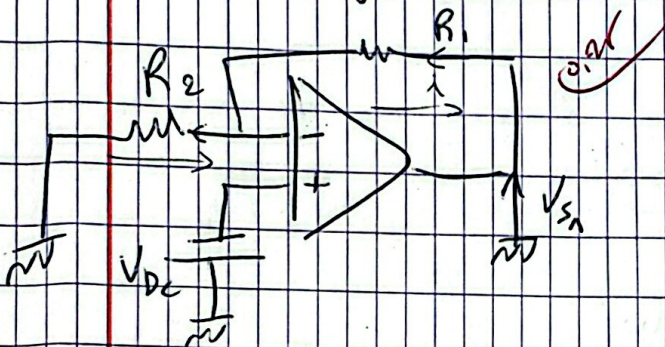
$V_{s1} = ?$ (in einem $V_{in} \rightarrow C \equiv \text{---}$)
on grade V_{DC}



$$V^+ = V^- = R_2 i = V_{DC} \Rightarrow i = \frac{V_{DC}}{R_2}$$

$$V_{s1} = (R_1 + R_2) i = \frac{(R_1 + R_2)}{R_2} V_{DC}$$

$V_{s2} = ?$

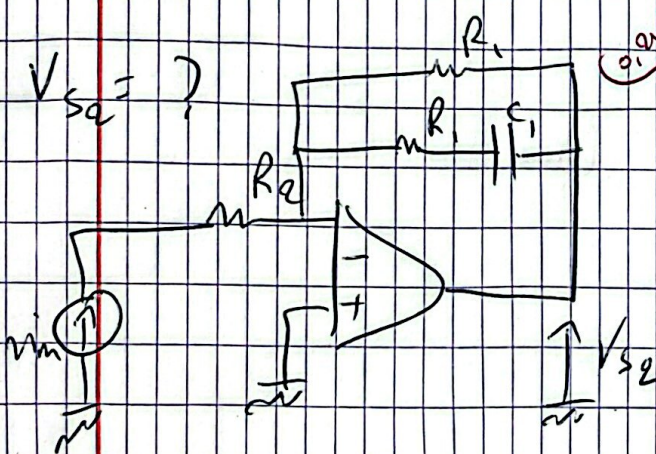

$$V_{s2} = - \frac{Z_1}{R_2} V_{in}$$

avec $Z_1 = R_1 // (R_1 + Z_{C1})$
 $= \frac{R_1 \times (R_1 + Z_{C1})}{R_1 + R_1 + Z_{C1}}$

$$= \frac{R_1 \times (R_1 + \frac{1}{j\omega C_1})}{2R_1 + \frac{1}{j\omega C_1}}$$

$$Z_1 = \frac{(R_1 + \frac{1}{j\omega C_1}) R_1}{j\omega C_1 R_1 + 1} = R_1 \left(\frac{1 + j\omega R_1 C_1}{1 + j\omega 2R_1 C_1} \right)$$



$$\rightarrow V_{s2} = - \frac{R_1}{R_2} \times \frac{(1+jR_1C_1\omega)}{(1+j2R_1C_1\omega)} V_{in}$$

$$\rightarrow V_s = V_{s1} + V_{s2} = \left(\frac{R_1+R_2}{R_2} \right) V_{in} + \frac{R_2}{R_2} \frac{(1+jR_1C_1\omega)}{(1+j2R_1C_1\omega)} V_{in}$$

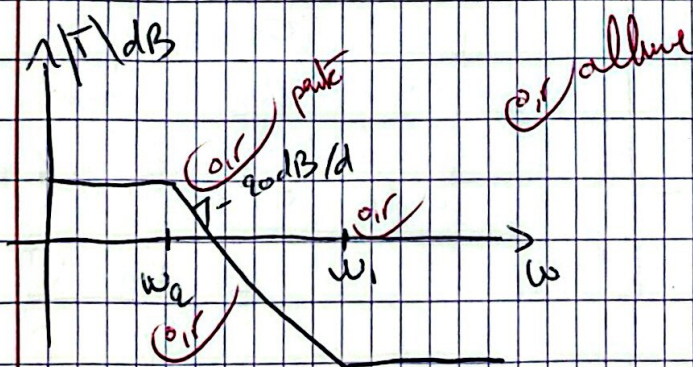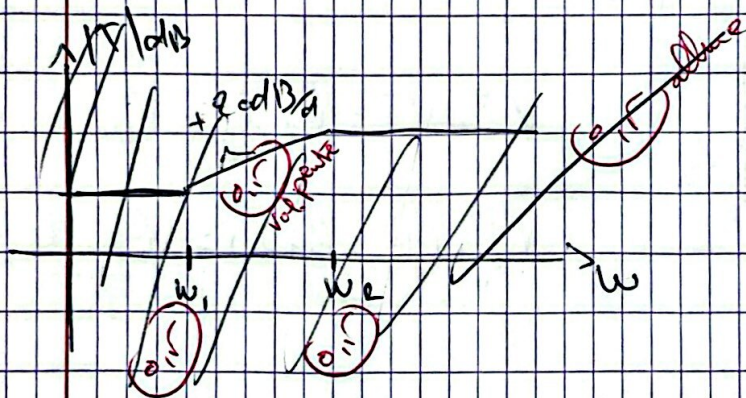2) $R_2 = \frac{R_1}{2}$ / $T(j\omega) = \frac{V_s}{V_{in}} = - \frac{R_1}{R_2} \left(\right)$

$$T(j\omega) = -2 \left(\frac{1+jR_1C_1\omega}{1+j2R_1C_1\omega} \right)$$

$$\omega_1 = \frac{1}{R_1C_1} \quad \text{or} \quad \omega_2 = \frac{1}{2R_1C_1} \quad 2R_1C_1 > R_1C_1$$



E x 4 :

$$G \times BP = 3 \pi H_z$$

on veut $gain_{total} = 900 \pm 5\%$ et $BP_{totale} = 300 kHz$

Etape 1 : $G_1 = \frac{3 \cdot 10^6}{300 \cdot 10^3} = 10$


$$BP_1 = 300 kHz \text{ (on impose)}$$

Etape 2 : $G_2 = \frac{gain_{total}}{G_1} = \frac{900}{10} = 90$

$$BP_2 = \frac{3 \cdot 10^6}{90} = 33,3 kHz \ll 300 kHz$$

→ non !

→ on fera donc 3 étages :

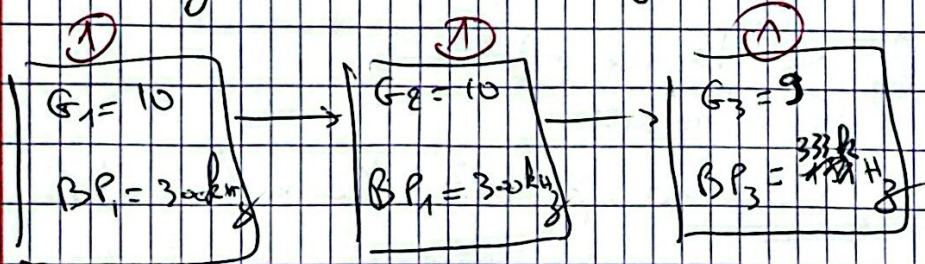

$$BP_3 = \frac{3 \cdot 10^6}{9} = 333 kHz$$

ampli 1 et 2 : $1 + \frac{R_2}{R_1} = 10 \Rightarrow \frac{R_2}{R_1} = 9$ (o.k.)

ampli 3 : $1 + \frac{R_2}{R_1} = 9 \Rightarrow \frac{R_2}{R_1} = 8$ (o.k.)

2) $V^+ = V_E$ et $V^- = R_1 i_1$

$V^+ = V^- \Rightarrow V_E = R_1 i_1 \Rightarrow i_1 = \frac{V_E}{R_1}$

pour que i^- soit négligeable devant i_1 , il faut que

$i^- \ll i_1 \Leftrightarrow i^- \ll \frac{V_E}{R_1} \Leftrightarrow i^- \ll \frac{V_{Emi}}{R_1} \Leftrightarrow R_1 \ll \frac{V_{Emi}}{i^-}$

$\Leftrightarrow R_1 \ll \frac{150 \cdot 10^{-6}}{3 \cdot 10^{-9}} \Leftrightarrow R_1 \ll 50 \text{ k}\Omega$

condition 2

$(R_1 + R_2) i_{smax} = V_{smax}$ or $V_{smax} = \text{gain} \times V_{inmax}$

~~$R_1 + R_2$~~ il faut que $i_s < i_{smax}$

$\frac{V_s}{R_1 + R_2} < 10 \text{ mA} \Leftrightarrow R_1 + R_2 > \frac{V_s}{10 \text{ mA}}$

$\Leftrightarrow R_1 + R_2 > \frac{V_{smax}}{10 \text{ mA}}$

or $\begin{cases} \text{AOP}_{1,2} : V_{smax} = 10 \times 2 \cdot 10^{-3} = 20 \text{ mV} \\ \text{AOP}_3 : V_{smax} = 9 \times 2 \cdot 10^{-3} = 18 \text{ mV} \end{cases}$

$\begin{cases} \text{AOP}_{1,2} : R_1 + R_2 > \frac{20 \text{ mV}}{10 \text{ mA}} (= 2 \Omega) \\ \text{AOP}_3 : R_1 + R_2 > \frac{18 \text{ mV}}{10 \text{ mA}} (= 1,8 \Omega) \end{cases}$

conclusion

AOP_{1,2}: on choisit $R_1 = 1 \text{ k}\Omega \Rightarrow R_2 = 9 \text{ k}\Omega$
AOP₃: $R_1 = 1 \text{ k}\Omega \Rightarrow R_2 = 8 \text{ k}\Omega$

Ex 2 (u)

$$E_{th} = e - v - v_1 = e - 2v = e - 2Ri \quad (1)$$

$$\text{or } E_{th} = R_3 i_3 = R_3 \left(gV + \frac{v}{R} \right) = R_3 v \left(g + \frac{1}{R} \right) \quad (2)$$

$$(1) \Rightarrow \cancel{v = E_{th}} \quad v = (e - E_{th})/2$$

$$\text{dans } (2) \Rightarrow E_{th} = R_3 \frac{(e - E_{th})}{2} \left(g + \frac{1}{R} \right)$$


$$\rightarrow E_{th} = \underbrace{\frac{R_3}{2} \left(g + \frac{1}{R} \right)}_{\alpha} (e - E_{th}) = \alpha e - \alpha E_{th}$$

$$\Leftrightarrow E_{th} (1 + \alpha) = \alpha e \rightarrow E_{th} = \frac{\alpha e}{1 + \alpha}$$

$$\rightarrow E_{th} = e \frac{\frac{R_3}{2} \left(g + \frac{1}{R} \right)}{1 + \frac{R_3}{2} \left(g + \frac{1}{R} \right)} = \frac{\frac{R_3}{2} \left(g + \frac{1}{R} \right) \times 2R}{\left(1 + \frac{R_3}{2} \left(g + \frac{1}{R} \right) \right) \times 2R} e$$

$$E_{th} = \frac{R_3 R g + R_3}{2R + R_3 R g + R_3} e \quad (1)$$

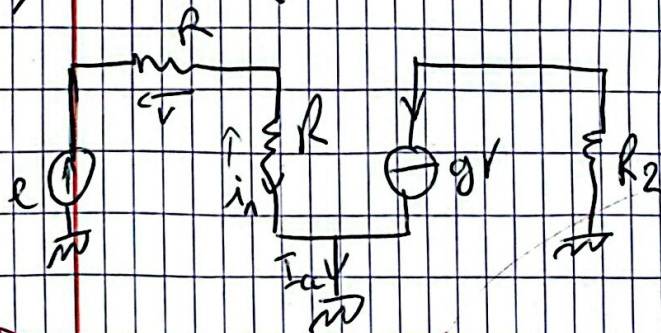e) R_{th} : (on CC la sortie) $\Rightarrow R_3$ en C.C



$$I_{cc} = gV + i_1 = gV + \frac{V}{R} = V \left(g + \frac{1}{R} \right) = \frac{e}{2} \left(g + \frac{1}{R} \right) = \frac{(gR + 1)}{2R} e \quad (1)$$

$$e = R i_1 + R i_n = V + V = 2V \Rightarrow V = \frac{e}{2}$$

$$\begin{aligned}
 \Rightarrow R_{rh} &= \frac{E_{rh}}{I_{cc}} = \frac{(R_3 R_g + R_3) \cancel{E}}{(R_3 R_g + R_3 + 2R)} \times \frac{2R}{\cancel{E} (1 + R_g)} \\
 &= \frac{\cancel{R_3} (R_g + 1) \cdot 2R}{\cancel{R_3} (R_g + 1 + \frac{2R}{R_3}) (1 + \cancel{R_g})} \\
 &= \frac{2R}{R (g + \frac{1}{R} + \frac{2}{R_3})} \\
 &= \frac{2}{\frac{R R_3 g + R_3 + 2R}{R R_3}}
 \end{aligned}$$

$$R_{rh} = \frac{2 R R_3}{R R_3 g + R_3 + 2R} \quad \textcircled{\wedge}$$

